

## Development of Virtual lab :Round 1 (R1) Pedagogy - Template (Worksheet)

**Name of Faculty:** Dr. Siddhartha Arjaria

**Institute:** Rajkiya Engineering College Banda

**Email ID** (as submitted in the registration form): arjarias@gmail.com

**Discipline to which the Lab belongs:** Electronics Engineering

**Name of the Lab:** Basic Electronics VLab

**Name of experiment :** Logic Gates

(only one Experiment per worksheet. for submitting more than one experiments, please fill up another worksheet):

**Kindly Refer these documents before filling the worksheet**

1. Coursework (MOOC ) on Pedagogy , Storyboard , Lab Manual : <http://bit.ly/Vlabs-MOOC>
2. Additional Documentation booklet for reference. <http://vlabs.iitb.ac.in/vlabs-dev/document.php>
3. Sample Git Repository. <https://github.com/Web-planner/Electronic-Simulator.git>

### 1.1 FOCUS AREA: Electronics Engineering Virtual Lab

#### 1.2 Logic gates simulator

#### 1.2 About the Experiment:

A **logic simulator** is a computer program that allows designers and experimenters to conduct virtual tests of complex digital circuitry before working with any hardware. ... Some programs also offer animation, signal tracing, and alternative **logic-gate** interconnection options.

#### 1.3 Learning Objectives: (write in the table below)

Write Learning Objectives that can be achieved using virtual labs and the respective cognitive level, & action verbs.

The objective for this lab is to understand the fundamentals of logic gates and its use in implementing basic Boolean functions.

### 4. Simulator Interactions

A **logic simulator** is a computer program that allows designers and experimenters to conduct virtual tests of complex digital circuitry before working with any hardware. The user **can** interact with the program to find a component arrangement that will perform a desired task.

## 5. Formula And Equations.

# • Logic Gates

## 1.. OR Gate

- Logic gates are electronic circuits that implement the basic functions of Boolean Algebra. There is a symbol for each gate

$$Z = A + B$$

A	B	Z
0	0	0
0	1	1
1	0	1
1	1	1

- Logic levels (0 or 1) are represented by means of a voltage level.
  - High voltage (5V, 3.3V, 2.5 V, etc.) is 1
  - Low voltage (0V) is 0

## 2. AND Gate

- Logic gates are electronic circuits that implement the basic functions of Boolean Algebra. There is a symbol for each gate

$$Z = A \cdot B$$

A	B	Z
0	0	0
0	1	0
1	0	0
1	1	1

- Logic levels (0 or 1) are represented by means of a voltage level.
  - High voltage (5V, 3.3V, 2.5 V, etc.) is 1
  - Low voltage (0V) is 0

### 3 . NOT Gate

- Logic gates are electronic circuits that implement the basic functions of Boolean Algebra.  
There is a symbol for each gate

$$Z = A$$

A	Z
0	1
1	0

- Logic levels (0 or 1) are represented by means of a voltage level.
  - High voltage (5V, 3.3V, 2.5 V, etc.) is 1
  - Low voltage (0V) is 0

### 4.NAND Gate

- Logic gates are electronic circuits that implement the basic functions of Boolean Algebra.  
There is a symbol for each gate

$$Z = A \cdot B = A + B$$

A	B	Z
0	0	1
0	1	1
1	0	1
1	1	0

- Logic levels (0 or 1) are represented by means of a voltage level.
  - High voltage (5V, 3.3V, 2.5 V, etc.) is 1
  - Low voltage (0V) is 0

### 5.NOR Gate

- Logic gates are electronic circuits that implement the basic functions of Boolean Algebra.  
There is a symbol for each gate

$$Z = A + B = A \cdot B$$

A	B	Z
0	0	1
0	1	0
1	0	0
1	1	0

- Logic levels (0 or 1) are represented by means of a voltage level.
  - High voltage (5V, 3.3V, 2.5 V, etc.) is 1
  - Low voltage (0V) is 0

## 6. XOR Gate

- Logic gates are electronic circuits that implement the basic functions of Boolean Algebra.  
There is a symbol for each gate

$$Z = A \oplus B = A \cdot B + A \cdot B$$

A	B	Z
0	0	0
0	1	1
1	0	1
1	1	0

- Logic levels (0 or 1) are represented by means of a voltage level.
  - High voltage (5V, 3.3V, 2.5 V, etc.) is 1
  - Low voltage (0V) is 0

## 7 . XNOR Gate

- Logic gates are electronic circuits that implement the basic functions of Boolean Algebra. There is a symbol for each gate

$$Z = A \oplus B = A \cdot B + A \cdot B$$

A	B	Z
0	0	1
0	1	0
1	0	0
1	1	1

- Logic levels (0 or 1) are represented by means of a voltage level.
  - High voltage (5V, 3.3V, 2.5 V, etc.) is 1
  - Low voltage (0V) is 0